
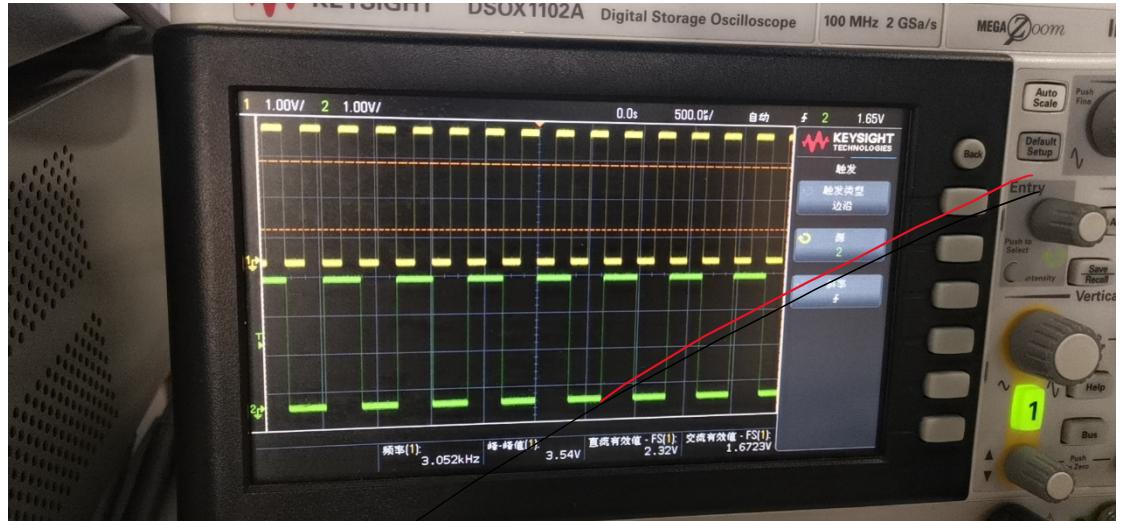


1. 十进制测量

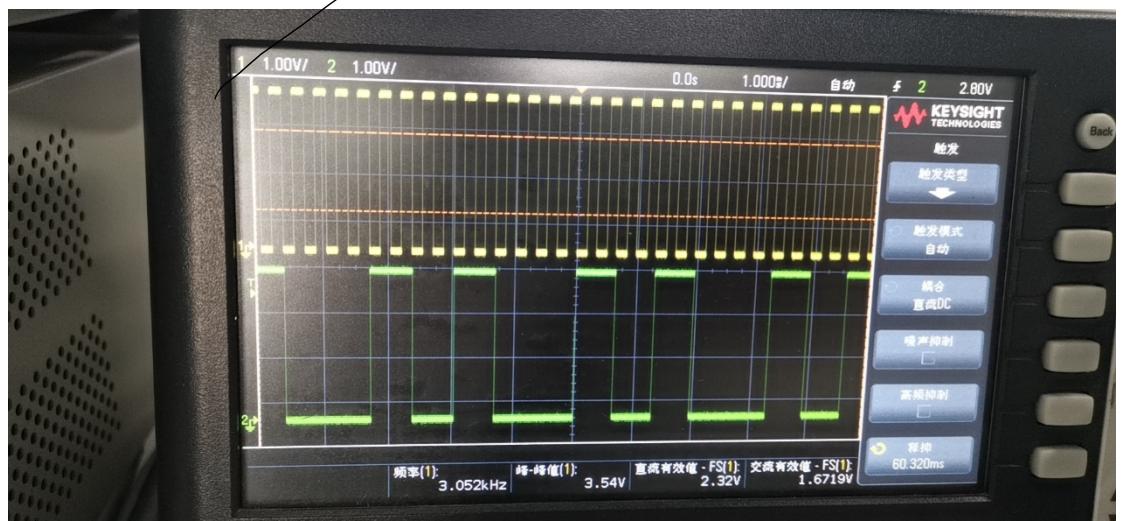- a) 通道一 (黄色): JB0 通道二 (绿色): 被测信号
- b) JB1




i. c) JB2



j. d) JB3




e) JB4

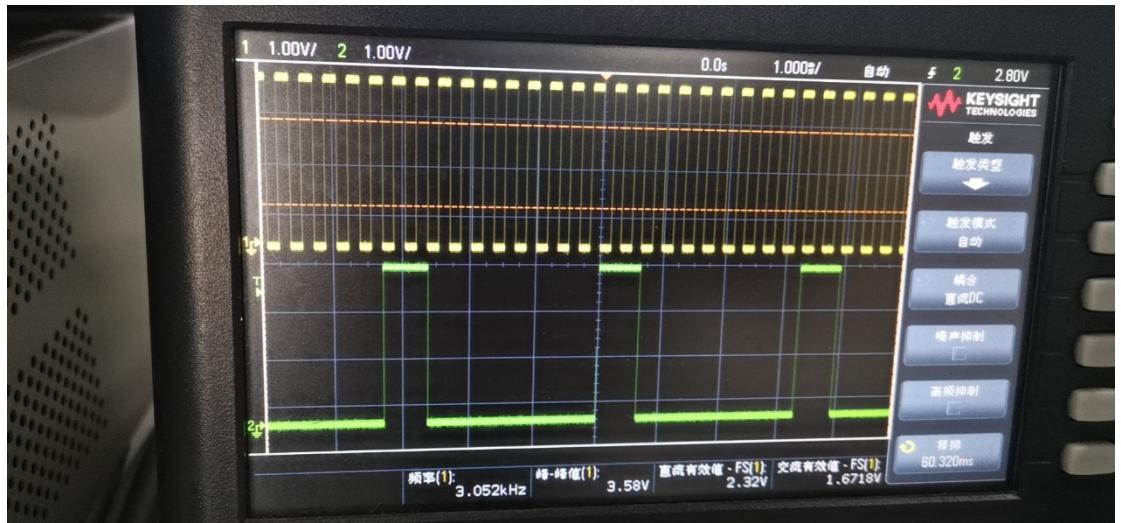


2. 十六进制测量

a) 通道一 (黄色): JB0 通道二 (绿色): 被测信号


b) JB1

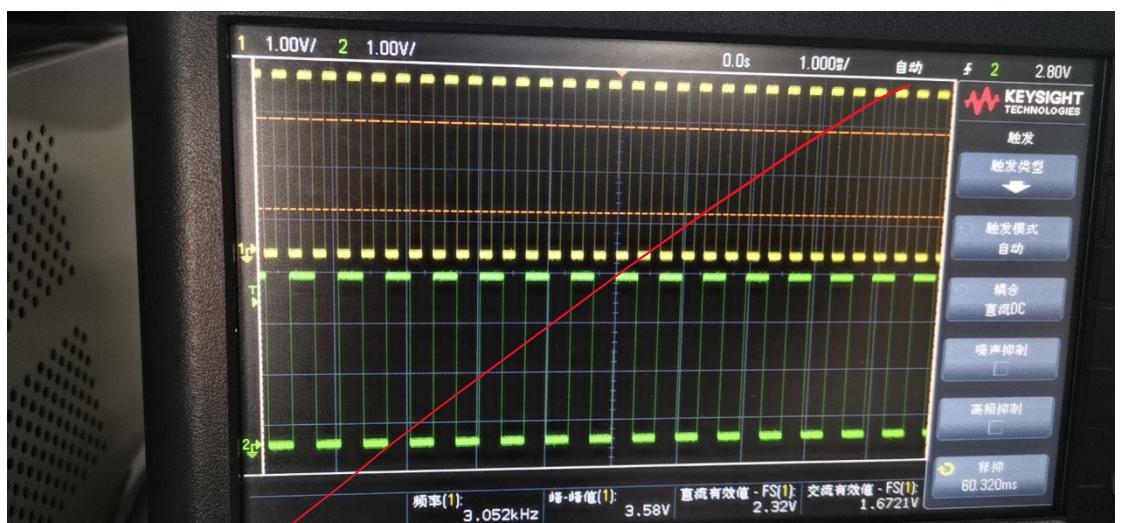

c) JB2

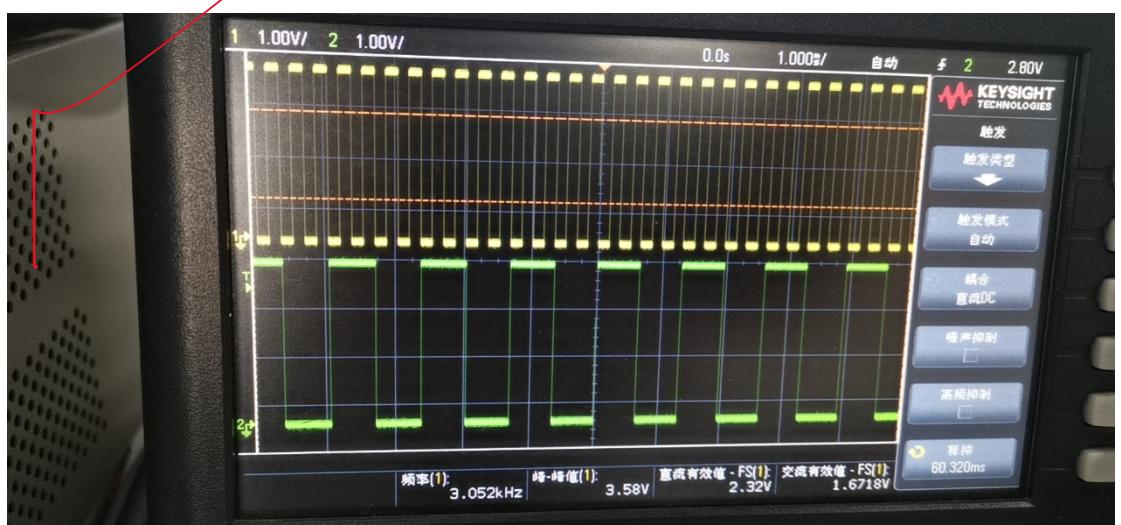


d) JB3

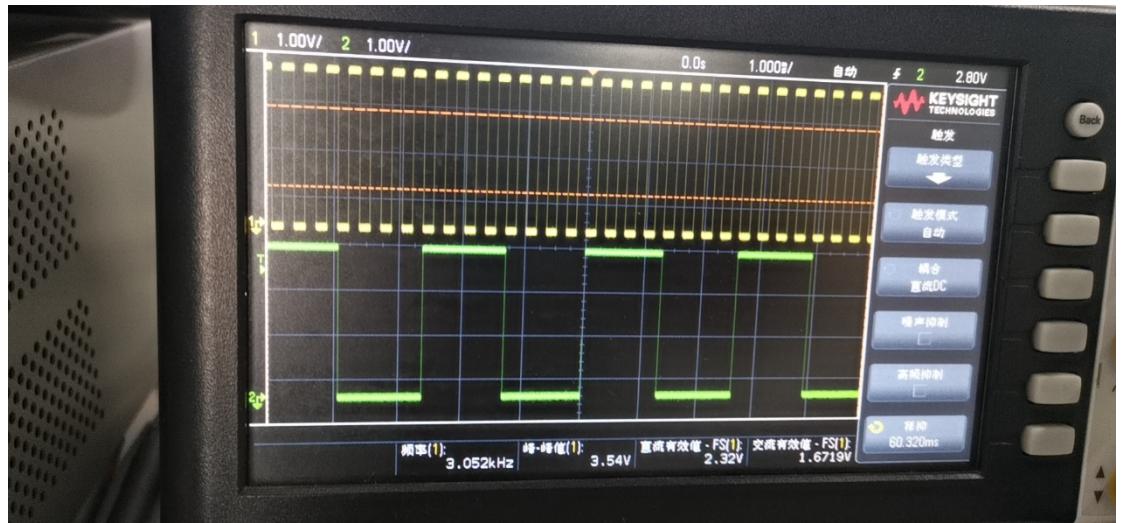

i.

e) JB4

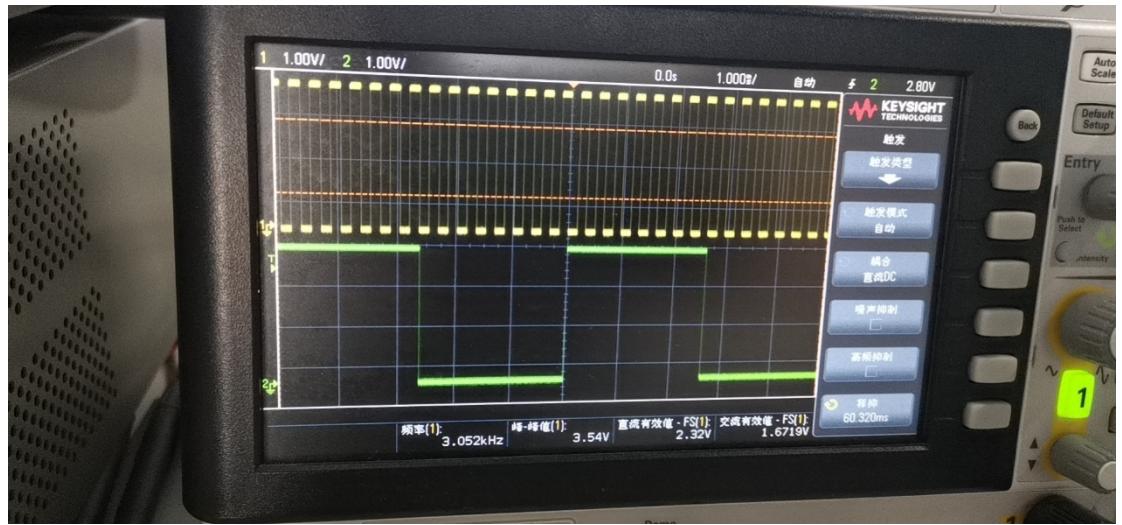


i.

3. 六进制测量 (置零法)


a) 通道一 (黄色): JB0 通道二 (绿色): 被测信号

b) 电路:

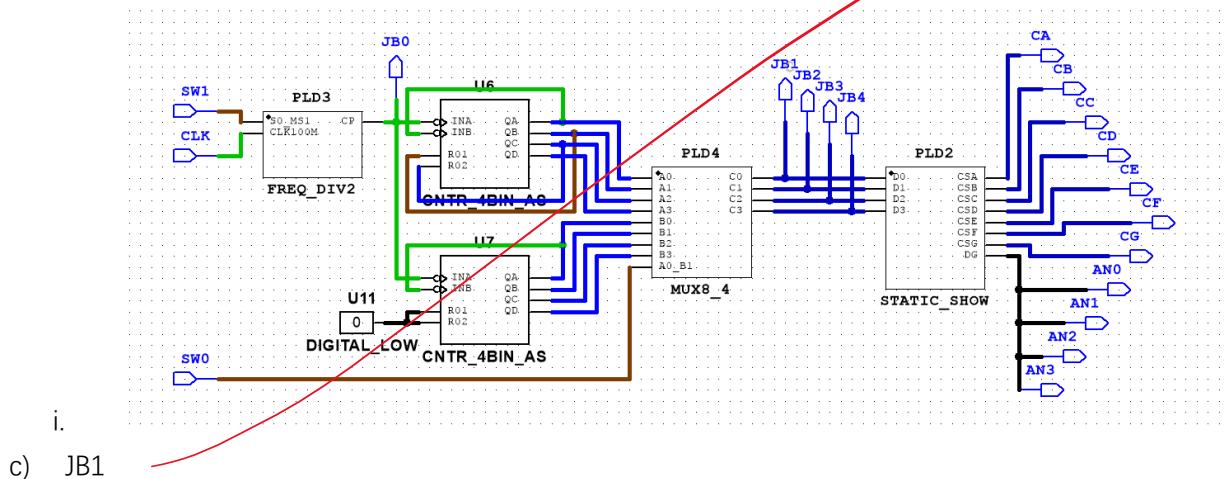


i.


c) JB1

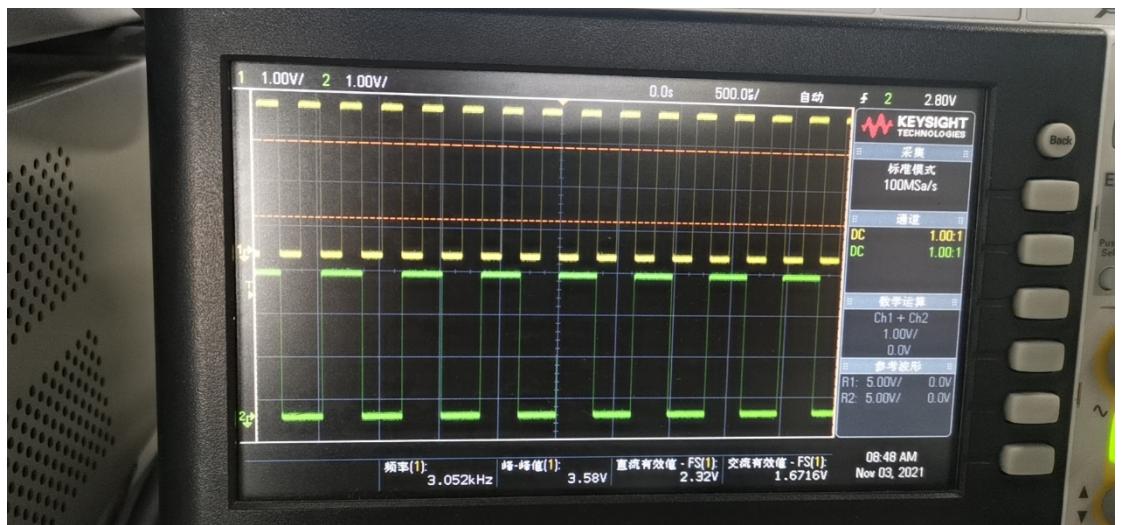


i) JB2

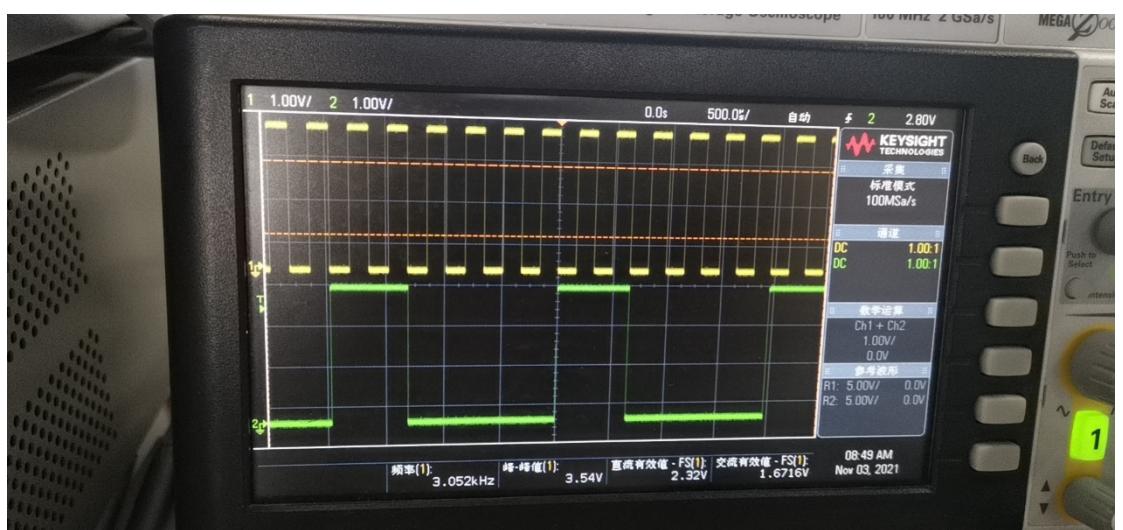

i) JB3

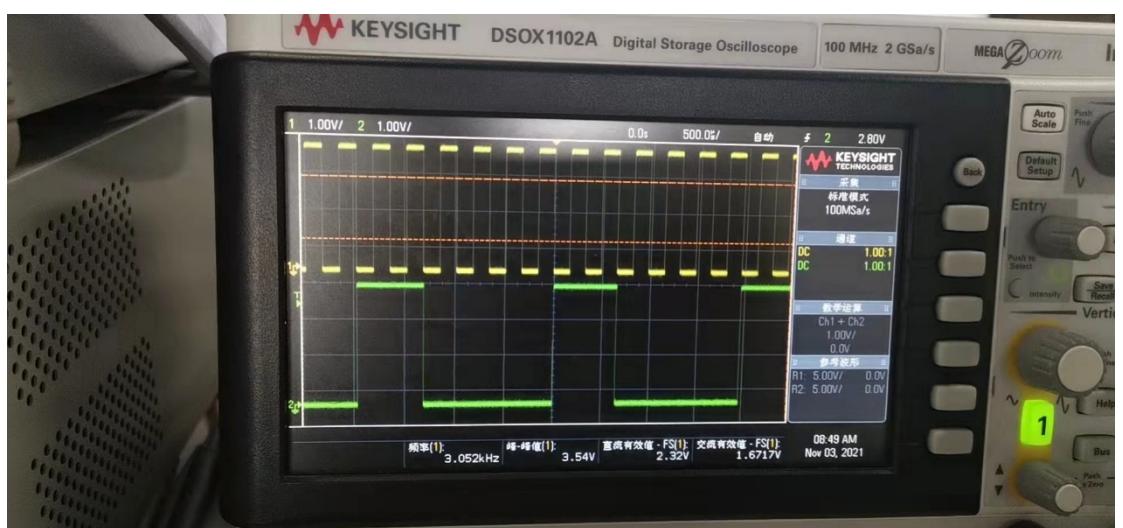


i) JB4

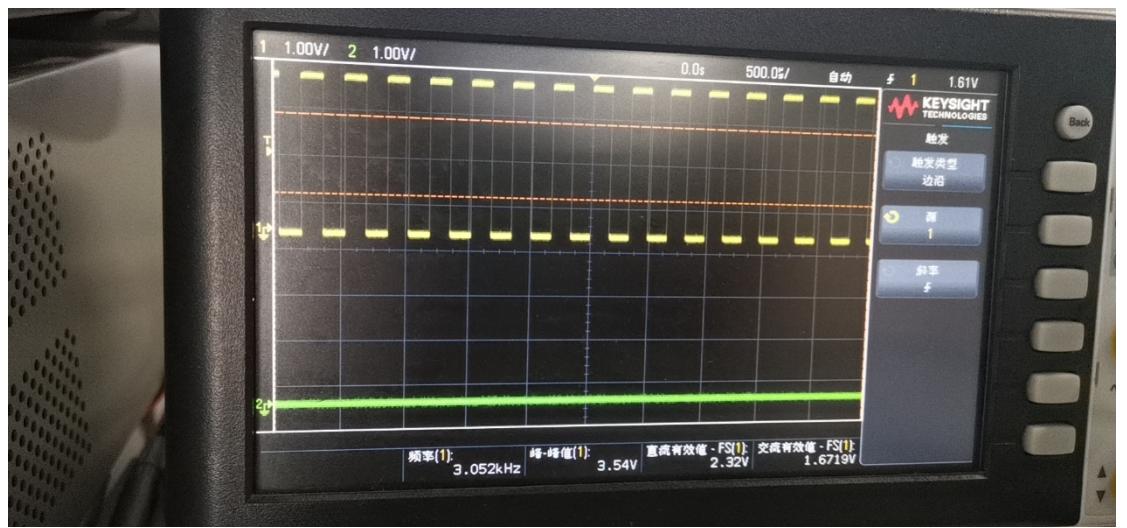





i. 4. 六进制测量 (置 9 法)

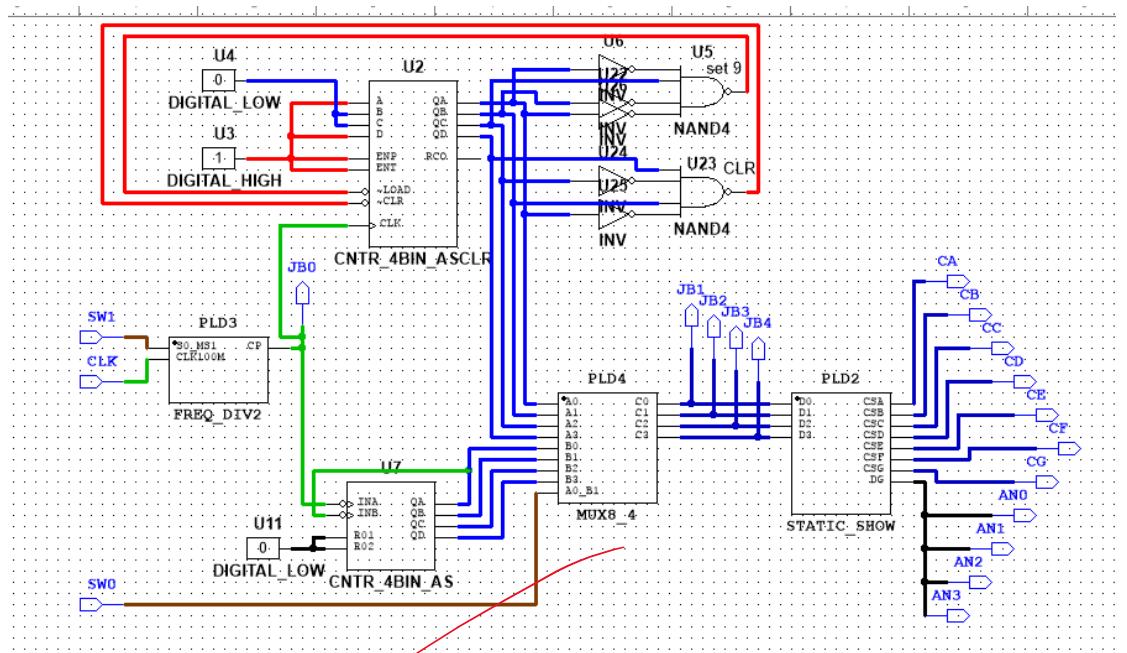
- a) 通道一 (黄色): JB0 通道二 (绿色): 被测信号
- b) 电路:



c) JB1

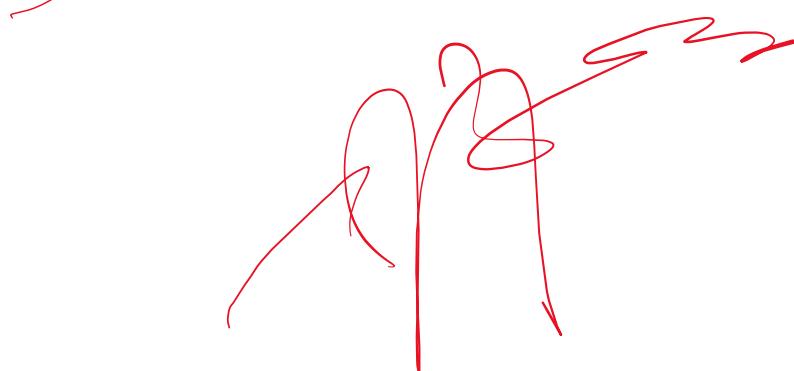

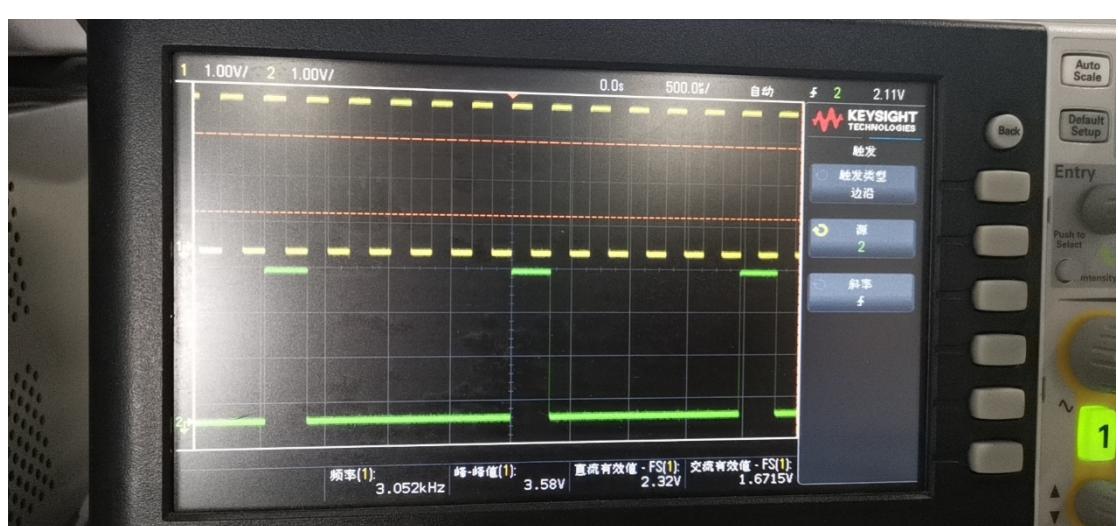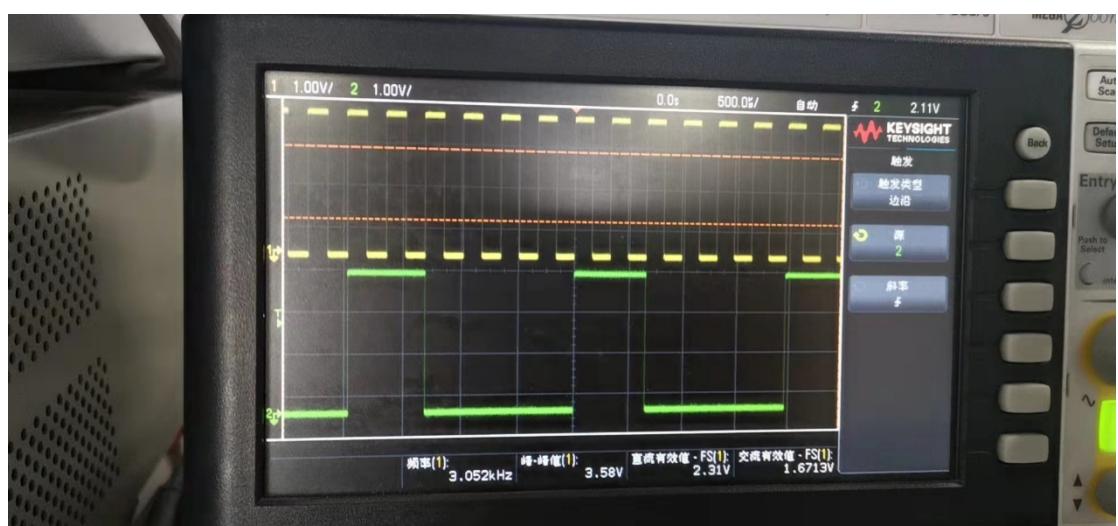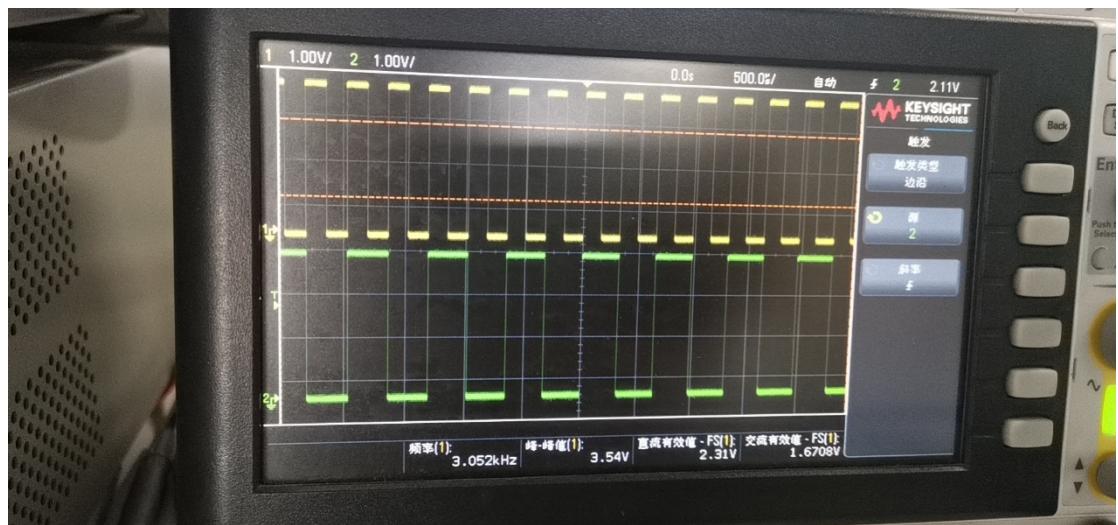

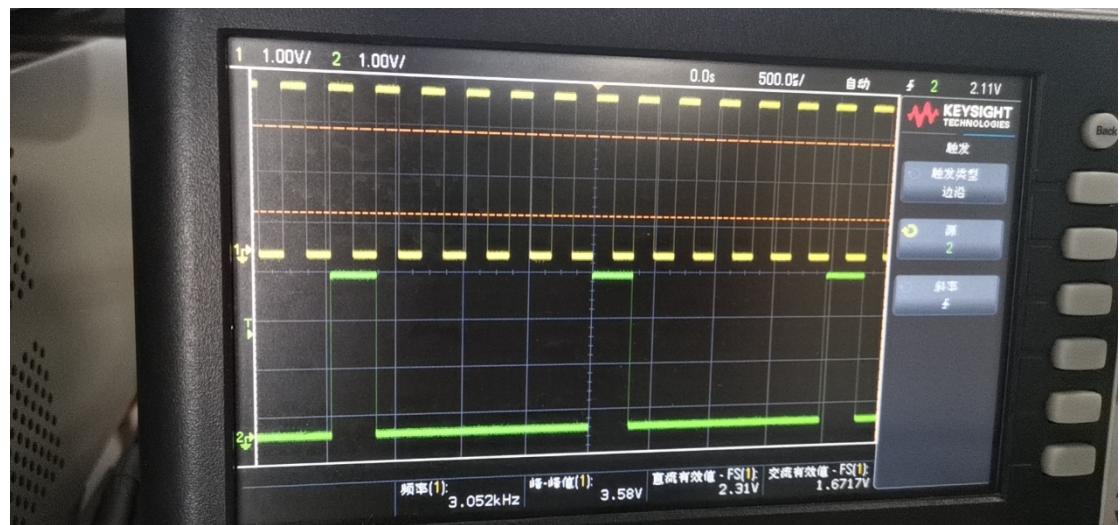

5.